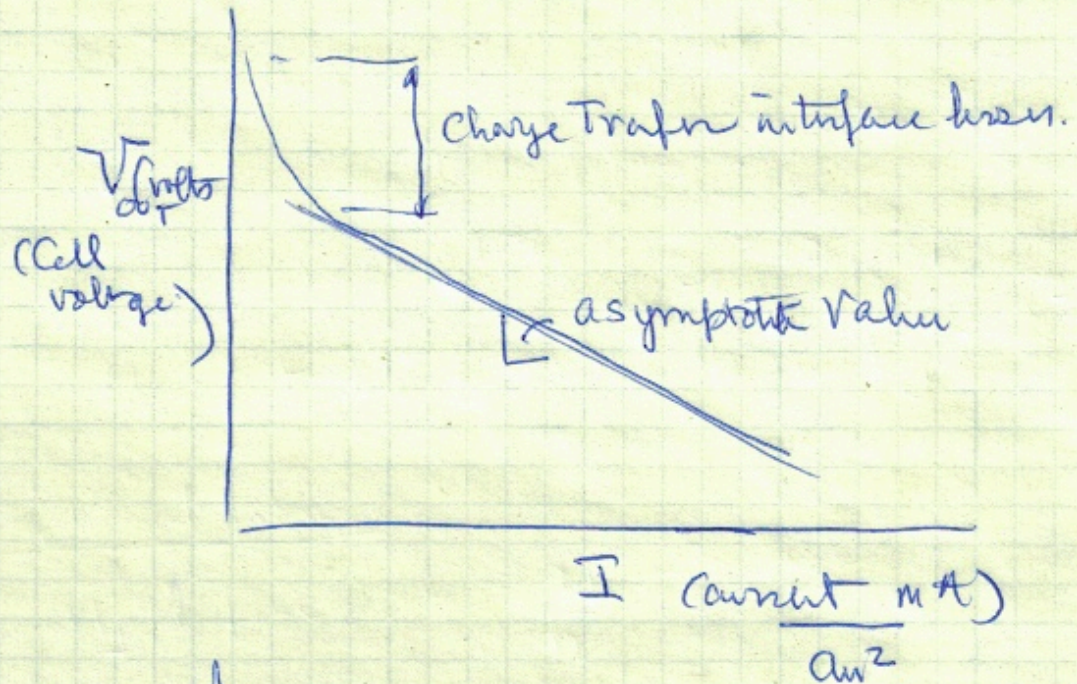



Analysis of the performance parameters in fuel cells.

Fuel Cell performance is characterized by the following two plots.

(i)




(ii)

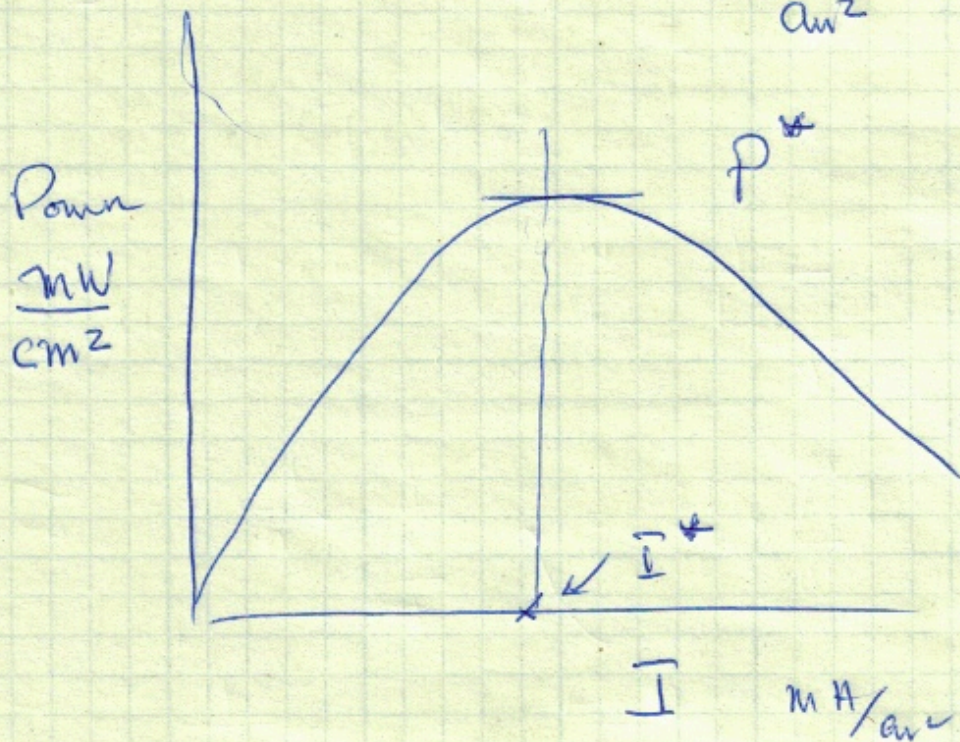

Note that current & power density are normalized with respect to the surface area of the cell.

In the following analysis we shall consider
 P in W and the current in A (but using
 the same nomenclature as in p.1)

Equivalent circuit -

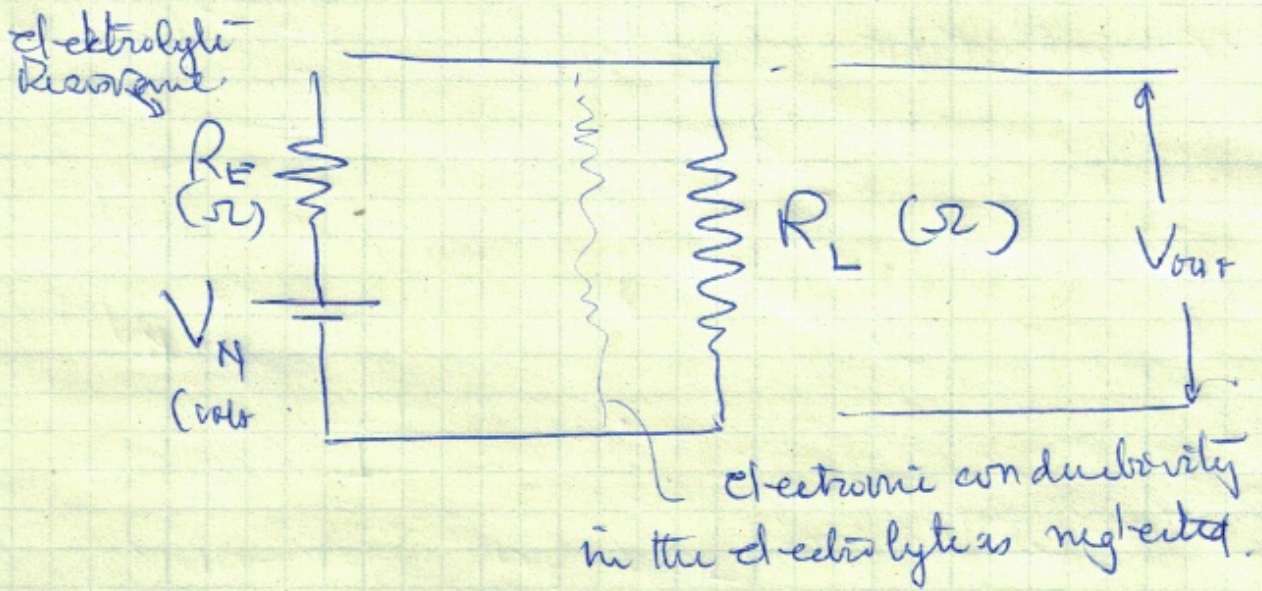

$$I = \frac{V_N}{R_E + R_L} \quad \text{--- ①}$$

$$V_{OUT} = V_N \times \frac{R_L}{R_E + R_L} \quad \text{--- ②}$$

Since I is controlled by reducing R_L with a c.c.f.t.,
 we need to eliminate R_L from ① & ②

$$\text{from ①} \quad R_L = \frac{V_N}{I} - R_E \quad \text{--- ③}$$

$$\text{for ③} \quad R_E + R_L = R_L \left[\frac{V_N}{V_{OUT}} \right]$$

$$R_L \left[\frac{V_N}{V_{out}} - 1 \right] = R_E$$

$$R_L = \frac{R_E}{\left[\frac{V_N}{V_{out}} - 1 \right]} \quad \text{--- (4)}$$

Eliminating R_L in ~~(1)~~ (3) & (4)


$$\frac{V_N}{I} - R_E = \frac{R_E}{\left[\frac{V_N}{V_{out}} - 1 \right]}$$

$$\frac{V_N}{I} = R_E \left[\frac{1}{\frac{V_N}{V_{out}} - 1} + 1 \right]$$


$$= R_E \times \frac{\frac{V_N}{V_{out}}}{\frac{V_N}{V_{out}} - 1}$$

$$I = \frac{1}{R_E} \times \frac{V_N \left[\frac{V_N}{V_{out}} - 1 \right]}{\frac{V_N}{V_{out}}}$$
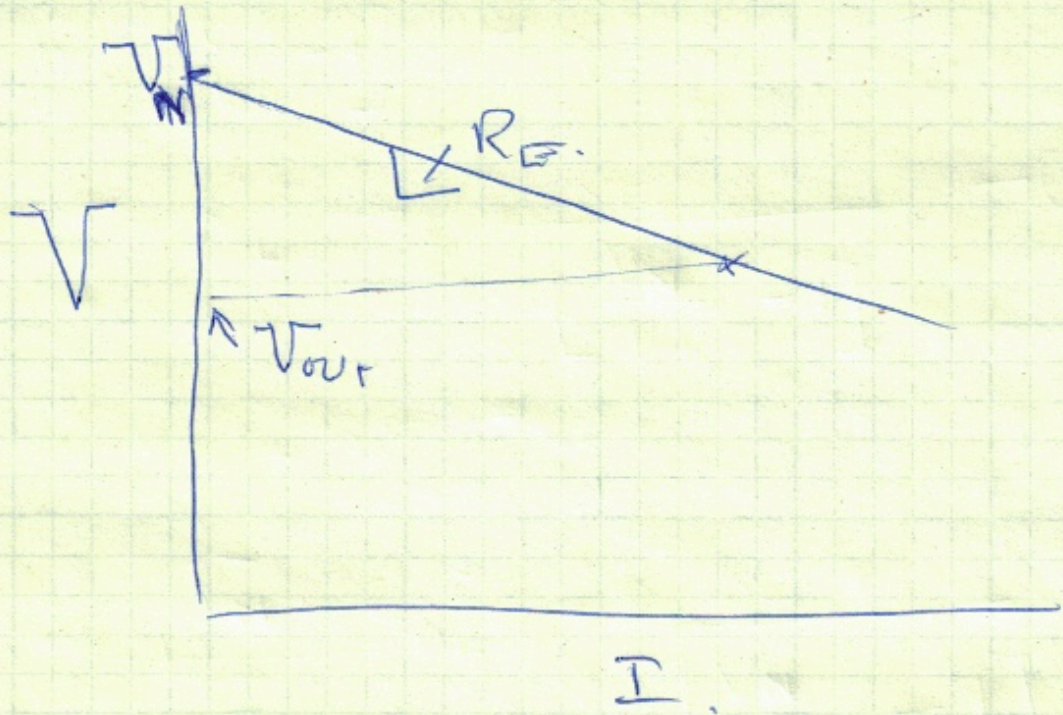
$$\therefore I = \frac{V_N - V_{out}}{R_E} \quad \text{--- (5)}$$



But because of interface effects

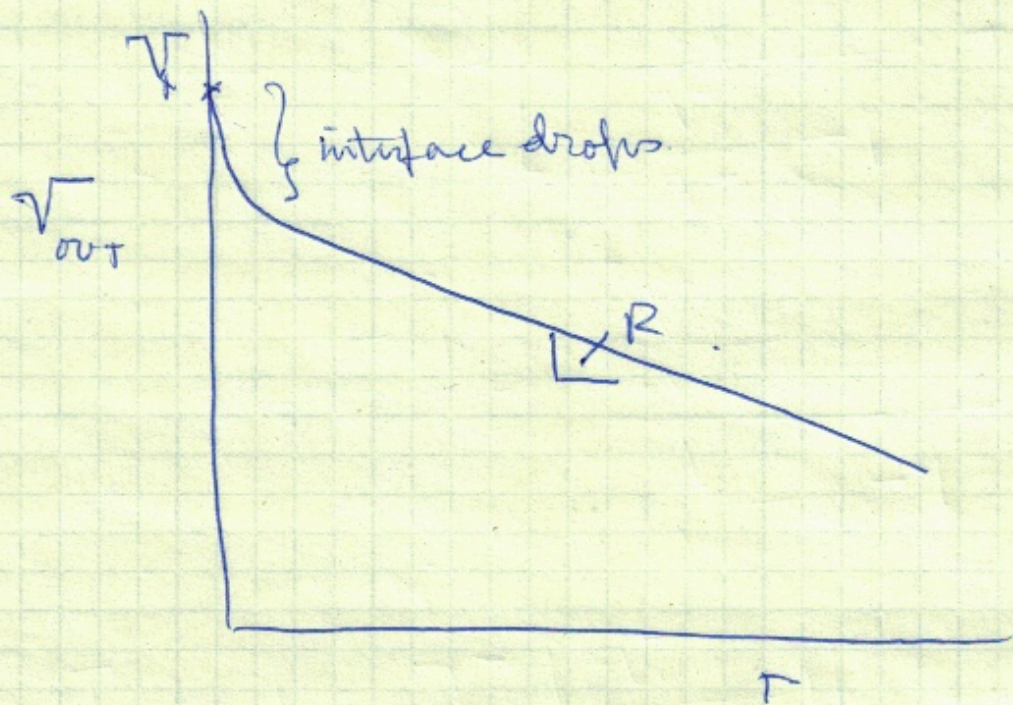

DEC 09 2019

$$\text{Power output} = V_{\text{OUT}} \times I$$

from Eq (5)

$$V_{\text{OUT}} = V_N - IR_E$$

$$P = IV_N - I^2 R_E \quad \text{--- (6)}$$

∴ To find the Max

$$\frac{dP}{dI} = V_N - 2IR_E^* = 0$$

$$\therefore I^* = \frac{V_N}{2R_E} \quad \text{--- (7)}$$

(6) + (7)

$$P^* = \frac{V_N^2}{2R_E} - \frac{V_N^2}{4R_E^2} \times R_E$$

$$P^* = \frac{V_N^2}{4R_E} \quad \text{--- (8)}$$

Note that Eqs (7) & (8) illustrate the great significance of R_E !